



UNIVERSITY OF WASHINGTON

BEE331 LAB 2

<i>2301991</i>	<i>2130474</i>
<i>Jason Truong</i>	<i>Henry Haight</i>

supervised by  
Prof. Joseph DECUIR

July 29, 2024

## MOSFET Bias Circuit

### Design Objective

In this lab we bias a MOSFET for use in both saturation and triode regions. This allows us to maintain a stable DC operating point.

### Circuit Design Outline

Using our calculated resistors of  $38.2k\Omega$  and  $95.3k\Omega$  combined with our given resistance values of  $500\Omega$  and  $1k\Omega$  and connecting them to our NMOS transistor in the configuration shown below we can bias our circuit so that the current across the  $500\Omega$  and  $1k\Omega$  ( $I_D$ ) is 10mA. By inputting a voltage of 15V at the leg of the  $500\Omega$  resistor we can achieve 10mA across the resistors.

## Measurement and Simulation Results

### Analysis

- **1. Calculate expected  $V_G$ ,  $I_D$  and  $V_{DS}$**

Given

- **2. Compare to simulated results for  $V_G$ ,  $I_D$  and  $V_{DS}$**

The simulated results for  $V_G$ ,  $I_D$  and  $V_{DS}$  all line up with what we observed during our measurements. The % difference between the calculated and simulated values were about

- **3. Comment on discrepancies**

### Summary & Conclusions